



AMPLIFICATORE DI RESISTENZA
by www.bbaba.altervista.org

$$iR3 = (Vin - Vu) / R3$$

$$Vu = Vin * R2 / (R1+R2)$$

$$iR3 = \{ Vin - [Vin * R2 / (R1+R2)] \} / R3$$

$$iR3 = Vin/R3 * [1 - R2 / (R1+R2)]$$

$$iR3 = Vin/R3 * [R1+R2 - R2 / (R1+R2)]$$

$$iR3 = Vin/R3 * [R1 / (R1+R2)]$$

$$Rin = Vin/iR3$$

$$Rin = Vin / \{ Vin/R3 * [R1 / (R1+R2)] \}$$

$$Rin = R3 * (R1+R2) / R1$$

$$A = (R1+R2)/R1$$

$$Rin = R3 * A$$

